



# İTÜ-EEF ANALOG ELECTRONIC CIRCUITS 2013

Prof. Dr. Melih Pazarıcı

## FINAL EXAM

Jan. 5, 2014

1)- The unloaded voltage gain of a given inverting amplifier is 100, and the input resistance  $r_i=15k\Omega$ . The amplifier is driven with a voltage source with an internal impedance of  $R_g$ . Load is  $R_L=10k\Omega$ .

a) The unloaded midband gain of the circuit is  $v_o/v_g=-60$ . When the load impedance  $R_L$  is connected to the output, the circuit gain drops to  $v_o/v_g=-48$ . Find  $R_g$  and the amplifier output resistance  $R_o$ .

b) The amplifier is connected to the source and load over coupling capacitors  $C_1$  and  $C_2$ , respectively. Find the  $C_1/C_2$  ratio so that  $f_{k2}=2f_{k1}$  for the associated low frequency poles.

c) Find  $C_1$  and  $C_2$  for a low frequency cutoff (-3dB) of 100Hz for the circuit.

Note: When poles are close  $f_k=(f_{k1}f_{k2}f_{k3}...)^{\frac{1}{n}}$  and  $f_L=\frac{f_k}{\sqrt{2^{\frac{1}{n}}-1}}$

$$\frac{f_{k1}}{f_{k2}}$$

d) Find the tilt at the output when a pulse with  $T_p=35\mu s$  is applied to the input (the pulse generator has the same  $R_g$ ). Note:  $\delta_T=\delta_1+\delta_2+...$

e) If the amplifier input capacitance  $C_i=40pF$ , output capacitance  $C_o=2pF$ , and the feedback capacitance is  $C_f=0.5pF$ , find the high frequency poles and the high cutoff frequency for the circuit (assume generator has the same  $R_g$ ). Note: Miller theorem: input  $(1-K)C_f$ , output  $(1-1/K)C_f$

f) A pulse with a rise time of  $0.1\mu s$  is applied to the input and the output rise time is measured using a scope with a rise time of  $0.1\mu s$ . Find the measured output rise time (the pulse generator has the same  $R_g$ ).

$$t_r = \frac{0.35}{f_H}, \quad t_r \approx \sqrt{t_1^2 + t_2^2 + ...}$$


2)- In the given circuit,  $|V_{BE}| \approx 0.7V$ ,  $V_T=25mV$ ,  $\beta_1=\beta_2=200$ ,  $\beta_3=500$ .

a) Find the value for  $R_2$  so that  $V_{C3Q}=0V$ .

b) Find the open loop midband gain of the circuit with  $\beta$  loading. What is the feedback topology?

c) Find  $v_o/v_i$  with feedback.

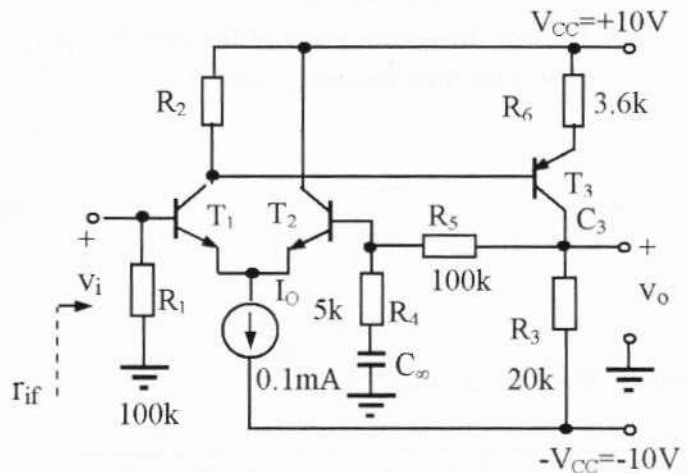d) Find  $v_o/v_g$  with feedback when the source resistance is  $R_g=40k\Omega$ .




Note: Diff. Amp. Single ended gain is

$$K_d = -\frac{R_{Leff}}{2r_e}$$

CONTINUED ON THE BACK- TURN OVER

$$C \frac{dV_C}{dt} = I_C$$

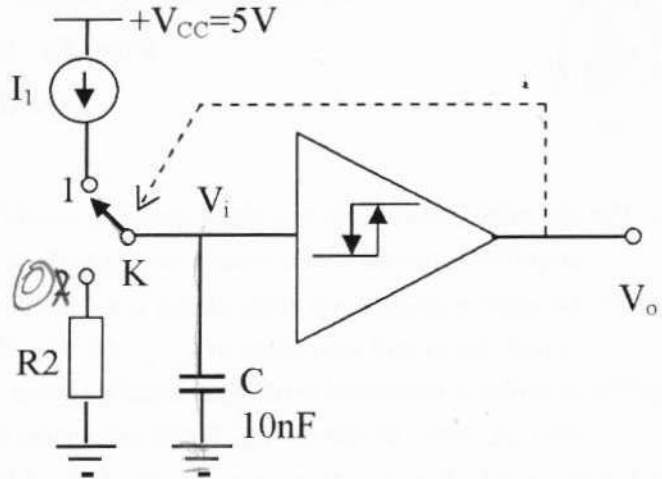
- 3)- In the relaxation oscillator given in the figure, the noninverting Schmitt circuit has:  $V_{IH}=3.5V$ ,  $V_{IL}=1.5V$ ,  $V_{OH}=5V$ ,  $V_{OL}=0V$ . Commutator switch K is connected to "1" when  $V_O$  is low, and to "0" when  $V_O$  is high.




- a)- Briefly describe the operation of the circuit.  
b)- For a square wave output (on/off ratio  $t_d/t_b=1$ ) with a frequency of 10kHz, find  $R_2$  and the current  $I_1$ . What does the on-off ratio depend on?  
c)- Design a suitable PNP current mirror current source for  $I_1$ . ( $|V_{BE}| \approx 0.7V$ )

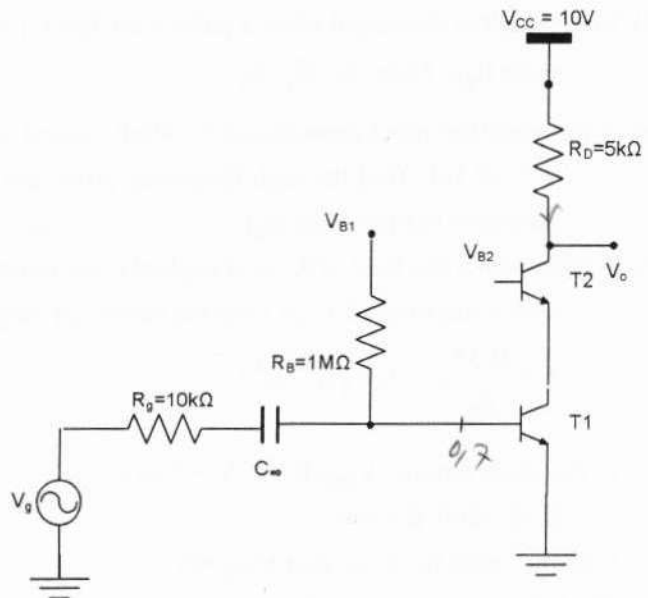- 4)- In the given circuit, T1 and T2 transistors are identical and both are biased in the forward conduction region.  $V_{BE}=0.7V$ ,  $\beta_F=100$ ,  $V_T=25mV$ ,  $h_{oe1} \approx 0$ ,  $h_{oe2} \approx 0$ ,  $C_{be1}=C_{be2}=20pF$ ,  $C_{cb1}=C_{cb2}=0.5pF$

- a)- Find  $I_{C1}$  for  $V_{B1}=5.7V$   
b)- Find the value range for  $V_{B2}$  for proper operation of the circuit.  
c)- Draw the small signal equivalent circuit and find the midband gain  $v_o/v_g$ .  
d)- Find the high frequency poles of the circuit. What is the high frequency cutoff?



$$h_{oe} = 1/r_{ce}$$

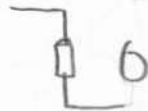

Hint: Do you recognize this circuit configuration!

Points: 30 + 30 + 20 + 20 = 100

Time 120".

**Notes:** Closed books & notes. No cellphones. You may make reasonable engineering approximations. All your approximations, roundings, and assumptions should be clearly visible. Be careful with your units.

ElektronDev2013\_Final.wpd