

①

a) $K_{Vo} = -100$ (@ $R_g = 0$ & $R_Y = \infty$)

When $R_g = R_Y = 10k\Omega \rightarrow \frac{V_o}{V_i} = K_{Vo} \cdot \frac{R_Y}{r_o + R_Y} = -80 \Rightarrow \boxed{r_o = 2,5k\Omega}$

$\frac{V_o}{V_g} = (-80) \cdot \frac{r_i}{R_g + r_i} = -48 \Rightarrow \boxed{r_i = 15k\Omega}$

b) $\omega_{k1} = \frac{1}{C_1 \cdot (R_g + r_i)} = \frac{1}{C_1 \cdot 25k}$, $\omega_{k2} = \frac{1}{C_2 \cdot (r_o + R_Y)} = \frac{1}{C_2 \cdot 12,5k}$

$\omega_{k1} = \omega_{k2} \Rightarrow \boxed{\frac{C_1}{C_2} = \frac{1}{2}}$ If $f_L = 70Hz \rightarrow \underbrace{f_{k1} = f_{k2}}_{\text{Double pole}} = f_L \cdot \sqrt{2} - 1 = 45,05Hz$

$f_{k1} = \frac{1}{2\pi C_1 \cdot 25k} = 45,05Hz \Rightarrow \boxed{\begin{matrix} C_1 = 141,3nF \\ C_2 = 282,6nF \end{matrix}}$

c) $\tau = \frac{1}{\omega_L} = 2,27ms \rightarrow$ For the tilt (δ): $\Delta V = V_m \cdot (1 - e^{-t/\tau})$
 $\frac{\Delta V}{V_m} = \delta = 1 - e^{-t/\tau} \leq 0,02$

$\Rightarrow t_d$: Pulse width, $1 - e^{-t_{dmax}/\tau} = 0,02 \rightarrow t_{dmax} = -\tau \cdot \ln(0,98)$

$\Rightarrow \boxed{t_d \leq 45,9\mu s}$

d) When $R_g = 0$, the pole contribution from $C_i \rightarrow \infty$

At the output side: $C_o' = C_o + (1 - \frac{1}{K}) \cdot C_\tau$ ($K = -100$)

$\omega_{k'} = \frac{1}{C_o' \cdot (r_o // R_Y)} = \frac{1}{C_o' \cdot 2k\Omega}$, $t_r = \frac{0,35}{f_{k'}} = 10ns \Rightarrow f_{k'} = 35MHz$
 $\rightarrow C_o' = 2,27pF$

$\Rightarrow \boxed{C_\tau = 267,3fF}$

When $R_g = 10k\Omega$: $\omega_{k1}' = \frac{1}{C_i' \cdot (R_g // r_i)}$, $C_i' = C_i + (1 - K) \cdot C_\tau$ ($K = -100$)
 $\rightarrow 6k\Omega$


$\omega_{k2}' = 35MHz$

$\rightarrow t_{r_{Tot}} = \sqrt{t_{r1}^2 + t_{r2}^2} = \sqrt{t_{r1}^2 + (10ns)^2} = 726ns \Rightarrow t_M = 725,9ns$

$t_{r1} = \frac{0,35}{f_{k1}'} = 725,9ns \Rightarrow f_{k1}' = 482,2kHz$

$f_{k1}' = \frac{1}{2\pi C_i' \cdot 6k} = 482,2kHz \Rightarrow C_i' = 55pF \rightarrow \boxed{C_i = 28pF}$

② Phase-shift network:

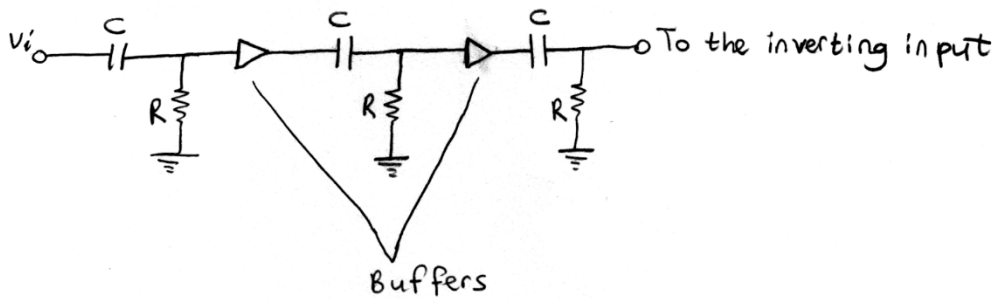

Since K_3 is an inverting opamp, this network should give a 180° of phase-shift. As they are buffered, each RC filter will have a 60° of phase-shift.

V_i — C — V — R — GND

$$\frac{V(s)}{V_i(s)} = H(s) = \frac{s}{s + \omega_k}, \text{ where } \omega_k = 1/RC$$

$$H(s)|_{s=j\omega} = H(\omega) = \frac{j\omega}{j\omega + \omega_k}$$

$$\begin{aligned} |H(\omega)| &= \sqrt{\frac{\omega^2}{\omega^2 + \omega_k^2}} \\ \angle H(\omega) &= 90^\circ - \tan^{-1}(\omega/\omega_k) \end{aligned}$$

At the oscillation frequency (ω_0):

$$\angle H(\omega)|_{\omega=\omega_0} = 90^\circ - \tan^{-1}(\omega_0/\omega_k) = 60^\circ \Rightarrow \omega_0 = \frac{\omega_k}{\sqrt{3}}$$

$$\Rightarrow \boxed{f_0 = \frac{1}{2\pi\sqrt{3}RC}}$$

$$|H(\omega)|_{\omega=\omega_0} = \sqrt{\frac{\omega_0^2}{\omega_0^2 + \omega_k^2}} = \sqrt{\frac{\omega_0^2}{\omega_0^2 + 3\omega_0^2}} = \frac{1}{2}$$

Since three stages are cascaded with buffers:


$$|H(\omega)|^3 = \frac{1}{8}$$

Then, $K_3 = -8 \rightarrow \boxed{R_2 = 8R}$

$$\textcircled{3} \quad K(s) = \frac{V_o}{V_i} = \frac{2\pi 10^7}{s + 2\pi 10^3} = K_o \cdot \frac{\omega_K}{s + \omega_K} \Rightarrow \omega_K = 2\pi 10^3 \text{ rad/s} \\ K_o = 10^4 \text{ (V/V)}$$


a) $K_o = 10^4 \text{ (V/V)}$

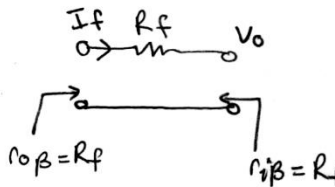b) Negative shunt-shunt f.b. (Genilinden akım g.b.)



$$\beta = \frac{I_f}{V_o} = \frac{-1}{R_f} = -1 \mu\text{S}$$

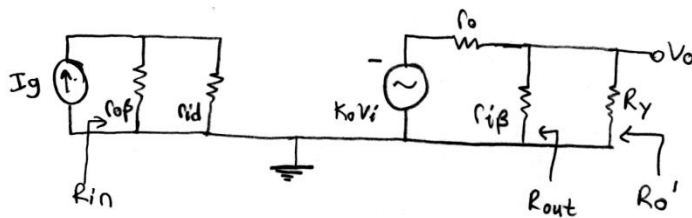→ Remove V_g and R_g , put an ideal current source I_g instead:




$$Z_m = \frac{V_o}{V_i} \cdot \frac{V_i}{I_g} = -K_o \cdot \frac{R_f \parallel r_{i\beta}}{r_o + R_f \parallel r_{i\beta}} \cdot (r_{o\beta} \parallel r_{id})$$

$$\Rightarrow Z_m = -606 \text{ M}\Omega$$

$$Z_{mf} = \frac{Z_m}{1 + \beta Z_m} \approx \frac{1}{\beta} = -1 \text{ M}\Omega \quad (1 + \beta Z_m = 607)$$

$$R_{in} = \frac{r_{o\beta} \parallel r_{id}}{1 + \beta Z_m} = 149,8 \Omega$$
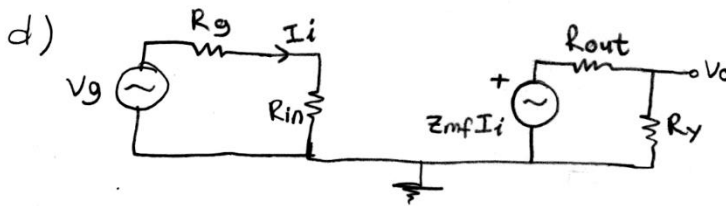
$$R_{o'} = \frac{R_f \parallel r_{i\beta} \parallel r_o}{1 + \beta Z_m} = 1,1 \Omega = R_{out} \parallel R_f \Rightarrow R_{out} \approx 1,1 \Omega$$



$$I_i = \frac{V_g}{R_g + R_{in}}$$

$$V_o = Z_{mf} \cdot I_i \cdot \frac{R_f}{R_{out} + R_f} \approx Z_{mf} I_i$$

$$\Rightarrow \frac{V_o}{V_g} = \frac{Z_{mf}}{R_g + R_{in}} = -868,3 \text{ (V/V)}$$

c) GBW product does not change w/ f.b.

→ w/o f.b. : $BW = 1 \text{ kHz}$, $G = 10^4 \rightarrow GBW = 10^7$

w/ f.b. : $G = -868,3 \Rightarrow BW = 11,5 \text{ kHz}$