

02/02/15 - W1

①

EHB 322E: Digital Electronic Circuits SPRING 2015

Course title

Electronics

low current
low voltage
small circuits
+ chips
+ Laptop, phones
(billions of transistors)

vs Electrical Engineering

high voltage
high current
large circuits
+ converters (AC-DC)
+ Power lines
+ Adapters

Electronics





Analog

old fashioned
you're so analog

Rx
Scale
Watch
Computer
(80% digital)

Digital

+ Modern

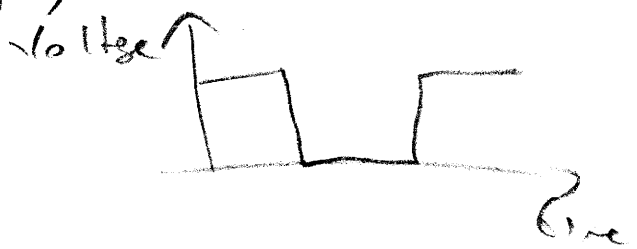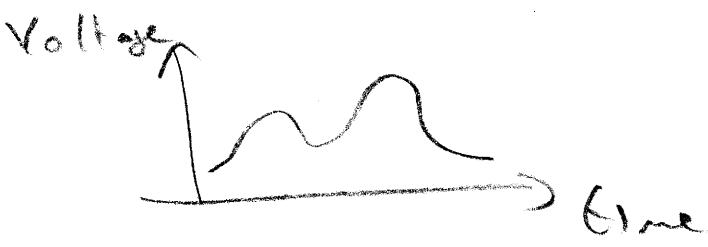

- Easier
- Noise sensitive

Essential

- easy to design
- more accurate
- we create it to make life easier (interface)

(2)

Digital Electronics

Transistor level

Gate level - System level

(Core: Digital Circuits)

- Mosfet

Metal-Oxide-Semiconductor

Field-Effect-Transistor

- CMOS Complementary (both NMOS and PMOS)

+ Analysis and Synthesis of MOSFET Level digital circuits

+ Performance parameters

- Power

- Area

- Delay (Speed)

- Reliability (non-emergencies)

Sensitivity

Ques Design a CMOS circuit implementing

$f = x_1 \bar{x}_2 + \bar{x}_1 x_2$ (XOR) with meeting

the specifications

+ W. Post Cox Dynamic Power Consumption $\leq 1 \text{ mW}$

+ Area $\leq 10 (\mu\text{m})^2$

+ max Delay $\leq 10 \text{ ns}$

Cost

$$f = x_1 \bar{x}_2 + \bar{x}_1 x_2$$

x_1	x_2	f
0	0	0
0	1	1
1	0	1
1	1	0

0 \rightarrow 0 Volt




1 \rightarrow 5 Volt

OR

0 \rightarrow -5V


1 \rightarrow +5V

Switches

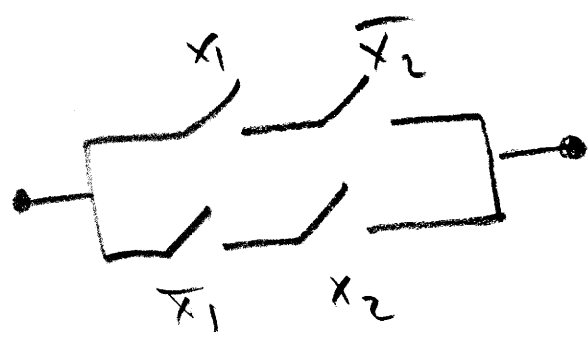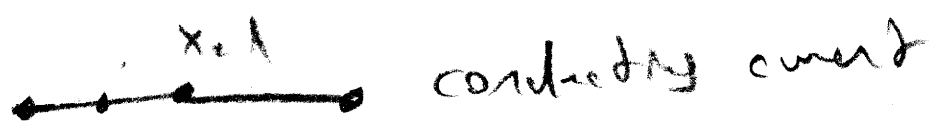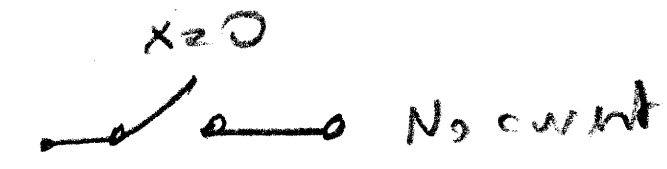


If there is a closed path between nodes then $f = 1$ otherwise $f = 0$

\downarrow NMOS

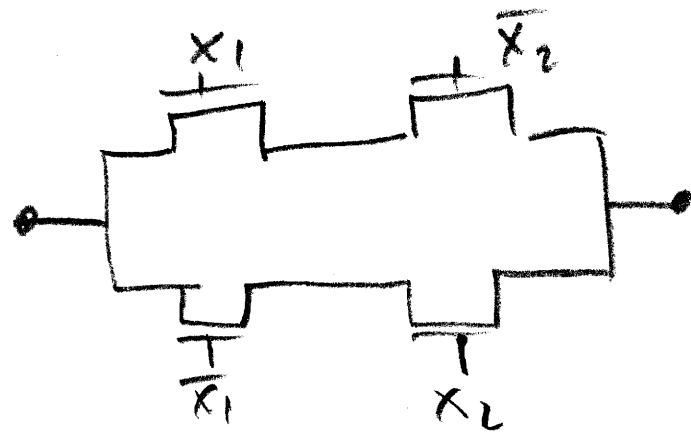

\downarrow PMOS

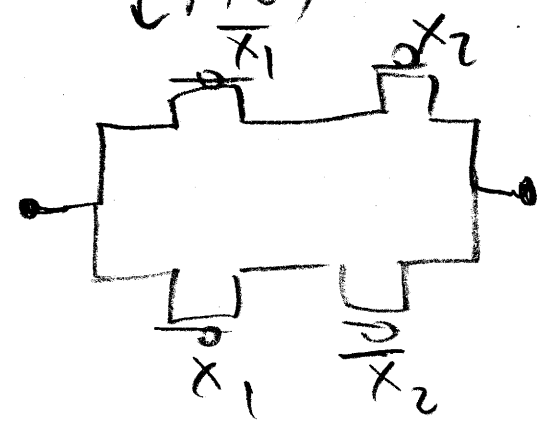

Course Website