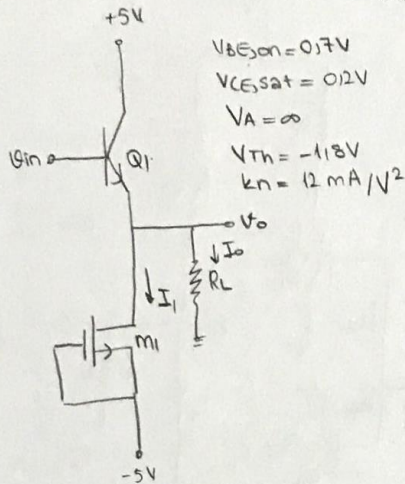


Enice BAYAL  
040170051



$$\begin{aligned} V_{BE, on} &= 0.7V \\ V_{CE, sat} &= 0.2V \\ V_A &= \infty \\ V_{TH} &= -1.8V \\ k_n &= 12 \text{ mA/V}^2 \end{aligned}$$

a) Determine  $V_{out, max}$  &  $V_{out, min}$  and the corresponding input voltages for the circuit operate in Class-A region for  
 $\rightarrow R_L = \infty$   
 $\rightarrow R_L = 500\Omega$ .

$$\begin{aligned} \text{When } V_{in} > V_{BE} &\rightarrow V_{out, max} = V_{CC} - V_{CE, sat} = 4.8V \\ \text{When } V_{in} < V_{BE} &\rightarrow \text{BJT is off} \rightarrow V_{out, min} = -I_D R_L \\ \rightarrow I_D = I_B &= 12 \cdot 10^{-3} \cdot (V_{GS} - V_T)^2 = 38.9 \text{ mA} \end{aligned}$$

for  $R_L = \infty$

$$V_{out, max} = V_{CC} - V_{CE, sat} = 4.8V$$

$$V_{in} - V_{out} = V_{BE} = 0.7V$$

$$V_{in} = 5.5V$$

$$V_{out, min} = -V_{CC} + V_{DS}$$

$$V_{DS} = V_{GS} - V_{TH} = 1.8V$$

$$V_{out, min} = -5 + 1.8V = -3.2V$$

$$V_{in} = 0.7 - 3.2V = -2.5V$$

for  $R_L = 500\Omega$

$$I_D = \frac{V_{out, min}}{R_L} = \frac{-3.2}{500} = -6.4 \text{ mA}$$

$$-6.4 \text{ mA} < 38.9 \text{ mA}$$

Therefore  $V_{out, max}$ ,  $V_{out, min}$  values are the same.

$$V_{out, max} = 4.8V$$

$$V_{out, min} = -3.2V$$

Q1 still derives!

b) What is the smallest value of  $R_L$  possible if a 2V peak sine wave is produced at the output?

$$P_{av} = (V_{CC} - V_{P2}) I_1 = V_{CC} I_1 - \frac{V_P^2}{2R_L} \quad | \quad V_P = I_1 R_L$$

$$4 \cdot I_1 = 5 I_1 - \frac{4}{2R_L}$$

$$R_L I_1 = 2V$$

$$R_L = \frac{2}{I_1} = \frac{2}{38.9 \times 10^{-3}} = 51.4 \Omega$$

c) What is the corresponding power conversion efficiency?

$$\eta = \frac{P_{L, av}}{P_{S, av}} \quad P_{L, av} = \frac{1}{T} \int_0^T \frac{(V_P \sin^2 \omega t)}{R_L} dt = \frac{V_P^2}{2R_L} = \frac{4}{2 \cdot 51.4} = 38.9 \text{ mW}$$

$$V_{out} = V_P \sin \omega t \quad P_{S, av} = \frac{1}{T} \int_0^T (V_{CC} - V_{EE}) \cdot I_1 dt = 10 \cdot 38.9 \text{ mA} = 389 \text{ mW}$$

$$\eta = \frac{38.9}{389} = 0.1 \rightarrow 10\%$$

- 2) Consider the class-AB output stage in Figure. Assume all transistors are matched, with parameters  $V_+ = V_- = 12V$  and  $\beta = 40$ ,  $V_{BE}(npn) = V_{BE}(pnp) = 0.7V$ ,  $R_1 = R_2 = 250\Omega$ ,  $R_3 = R_4 = 0.2\Omega$ ,  $R_L = 8\Omega$

a) For  $V_i = 0V$  determine  $i_{E1}$ ,  $i_{E2}$ ,  $i_{B1}$  &  $i_{B2}$ .

$$V_i = 0 \Rightarrow V_{B1} = V_{B2} = 0V$$

$$\alpha = \frac{\beta}{1+\beta} = \frac{40}{41}$$

$$12 - R_1(i_{E1} + i_{B3}) = 0.7V$$

$$-V_{E1} - V_{BE} = 0.7V$$

$$V_{E1} = +0.7V \quad V_{E2} = -0.7V$$


$$\frac{-0.7 - (-12)}{R_2} = i_{E2} - i_{B4}$$

$$V_i = 0 \Rightarrow V_o = 0 \Rightarrow i_o = 0 \Rightarrow i_{E3} = i_{E4} \quad i_1 = 0 \Rightarrow i_{B1} = i_{B2} \quad i_{E1} = i_{E2}$$

$$12 - 250(i_{E1} + i_{B3}) = 0.7V$$

$$\frac{11.3}{250} = i_{E2} - i_{B4} \quad \left\{ \begin{array}{l} i_{E1} = i_{E2} = 45.2 \text{ mA} \\ i_{B1} = i_{B2} = \frac{45.2 \times 10^{-3}}{41} \approx 1.1 \text{ mA} \end{array} \right.$$

$$\frac{11.3}{250} = i_{E2} + i_{B4}$$

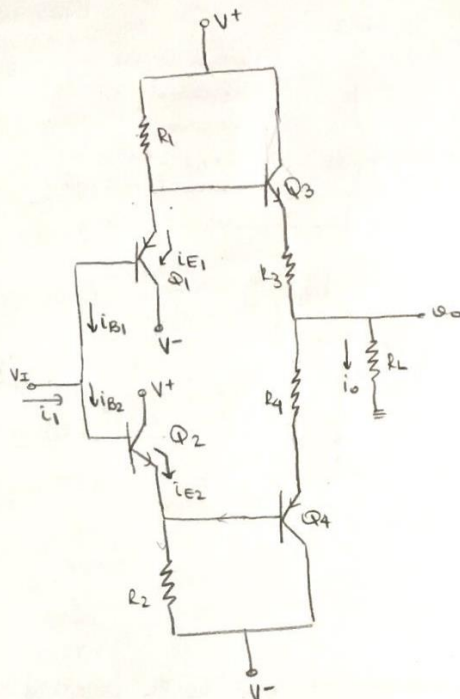

b) For  $V_i = 5V$  determine  $i_1$ ,  $i_o$ ,  $i_{E1}$  &  $i_{E2}$ ,  $i_{B1}$  &  $i_{B2}$ .

$$V_i = 5V = V_{B1} = V_{B2}$$

$$V_{B3} = V_{E1} = 5.7V \rightarrow V_{E3} = V_{B3} - 0.7 = 5V = V_o \quad \left. \begin{array}{l} V_{B4} = V_{E2} = 4.3V \rightarrow V_{E4} = 5V = V_o \end{array} \right\} R_3 = R_4 = 0.2\Omega$$

$$V_o = 5V \Rightarrow \frac{V_o}{R_L} = i_o = \frac{5}{8} = 625 \text{ mA}$$

$$i_o + i_{E4} = i_{E3} \rightarrow i_{B3} \cdot \beta$$

$$i_{B4} \cdot \beta$$

$$41(i_{B3} - i_{B4}) = 625 \times 10^{-3} \text{ A}$$

$$i_{B3} - i_{B4} = 0.015244 \text{ A}$$

$$i_{E3} - i_{E4} = 0.015 \times 41 \approx 0.625 \text{ A}$$

$$\text{if we assume } i_{E3} = i_o = 0.625 \text{ A}$$

$$i_{B3} = \frac{1}{41} \cdot 0.625 = 15.244 \text{ mA}$$

$$i_{E1} = 9.956 \text{ mA} \quad i_{B1} = 242.83 \mu\text{A}$$

$$i_{E2} = 6.12 \text{ mA} \quad i_{B2} = 1.6 \text{ mA}$$

$$i_o = 625 \text{ mA} \quad i_{in} = 1.3474 \text{ mA}$$

$$+ \frac{V_{B4} - (-12)}{R_2} = i_{B4} = i_{E2} \rightarrow + (i_{E2} + i_{B4}) \cdot R_2 = 4.3 + 12$$

$$i_{E2} + i_{B4} = 0.0652$$

$$+ \frac{12 - V_{B3}}{R_1} = i_{B3} + i_{E1} \rightarrow + i_{B3} + i_{E1} = 0.0252$$

$$i_{E2} - i_{E1} = 0.004 + (i_{B3} - i_{B4})$$

$$= 0.04 + 0.015244$$

$$= 0.055244$$

$$i_{E1} = i_{B2} - i_{B1} = \frac{1}{41} \cdot 0.055244$$

$$= 1.3474 \text{ mA}$$

c) Current gain = ?

$$\frac{i_o}{i_{in}} = \frac{0.625}{1.3474 \times 10^{-3}} = 463.856316$$



3

Consider the class-AB MOSFET output stage in Figure.

$I_{bias} = 0.2 \text{ mA}$ ,  $R_L = 1 \text{ k}\Omega$ ,  $V_{TH,n} = 0.8 \text{ V}$ ,  $k'_n = 100 \mu\text{A/V}^2$ ,  $V_{TH,p} = -0.8 \text{ V}$ ,  $k'_p = 40 \mu\text{A/V}^2$

For the quiescent condition, assume  $V_{GS,3} = V_{GS,4}$ ,  $\lambda = 0$  for all transistors.

$V_{GS,1} = V_{GS,2}$

a) If  $V_i = -1.5 \text{ V}$ ,  $V_o = 0 \text{ V}$ ,  $i_{D1} = i_{D2} = 0.15 \text{ mA}$ ; determine  $W/L$  ratios.

$$\begin{aligned} V_i = -1.5 \text{ V} &\Rightarrow V_{S2} = 0 \text{ V} \\ V_o = 0 \text{ V} &\Rightarrow V_{G2} = V_{D4} = V_i = -1.5 \text{ V} \\ &\Rightarrow V_{SG2} = V_{GS1} = 1.5 \text{ V} \end{aligned}$$

$$i_{D1} = i_{D2} = 0.15 = \frac{0.1}{2} \left( \frac{W}{L} \right)_1 \underbrace{(V_{GS1} - V_{TH,n})^2}_{(1.5 - 0.8)^2} = 0.49$$

$$\left( \frac{W}{L} \right)_1 = 20.411$$

$$0.15 = \frac{0.104}{2} \left( \frac{W}{L} \right)_2 \cdot 0.49$$

$$\left( \frac{W}{L} \right)_2 = 51 //$$

$$\Rightarrow V_{G4} = V_i \quad V_{G3} = V_{G1} = 1.5 \text{ V} \\ V_{S4} = V_{S3}$$

$$V_{G3} - V_{S3} = V_{S4} - V_{G4}$$

$$1.5 - V_{S3} = V_{S3} + 1.5$$

$$V_{S3} = V_{S4} = 0$$

$$V_{GS3} = V_{GS4} = 1.5 \text{ V}$$


$$I_{bias} = 0.2 = \frac{0.1}{2} \left( \frac{W}{L} \right)_3 (1.5 - 0.8)^2$$

$$1 = \left( \frac{W}{L} \right)_3 \cdot 0.49$$

$$\left( \frac{W}{L} \right)_3 = 8.16 //$$

$$0.2 = \frac{0.104}{2} \cdot \left( \frac{W}{L} \right)_4 \cdot 0.49$$
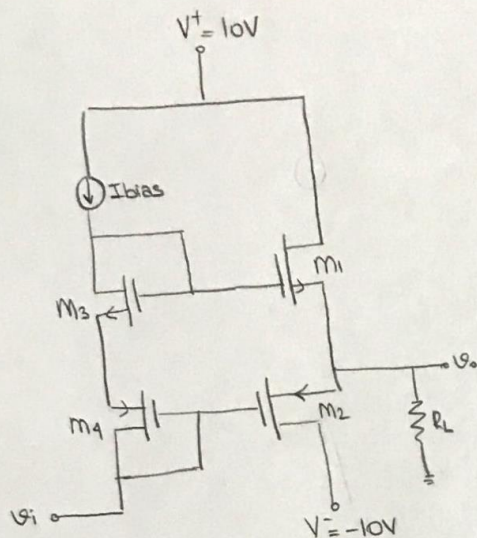
$$\left( \frac{W}{L} \right)_4 = 20.4 //$$



b) Assuming voltage drop across  $I_{bias}$  of  $0.2 \text{ V}$ ,  $V_i = -1.5 \text{ V}$ , find the max. and min. limits of  $V_o$ .

$$V_{omax,1} = V^+ - V_{ov(bias)} - V_{GS1} = 10 - 0.2 - 1.5 = 8.3 \text{ V}$$

$$V_{omax,2} = V^+ - V_{DS,1} = 10 - 0.7 = 9.3 \text{ V} //$$

$$\rightarrow V_{GS} - V_{TH} = 0.7$$


$$V_{omin,1} = V^- + |V_{SD,2}| = -8.3 \text{ V}$$

$$V_{omin,2} = V_{ov(in)} + |V_{SG,2}| = 0$$


$$0 \leq V_o \leq 8.3 \text{ V} //$$

## Question 4

### a) When $R = 8\text{ ohms}$

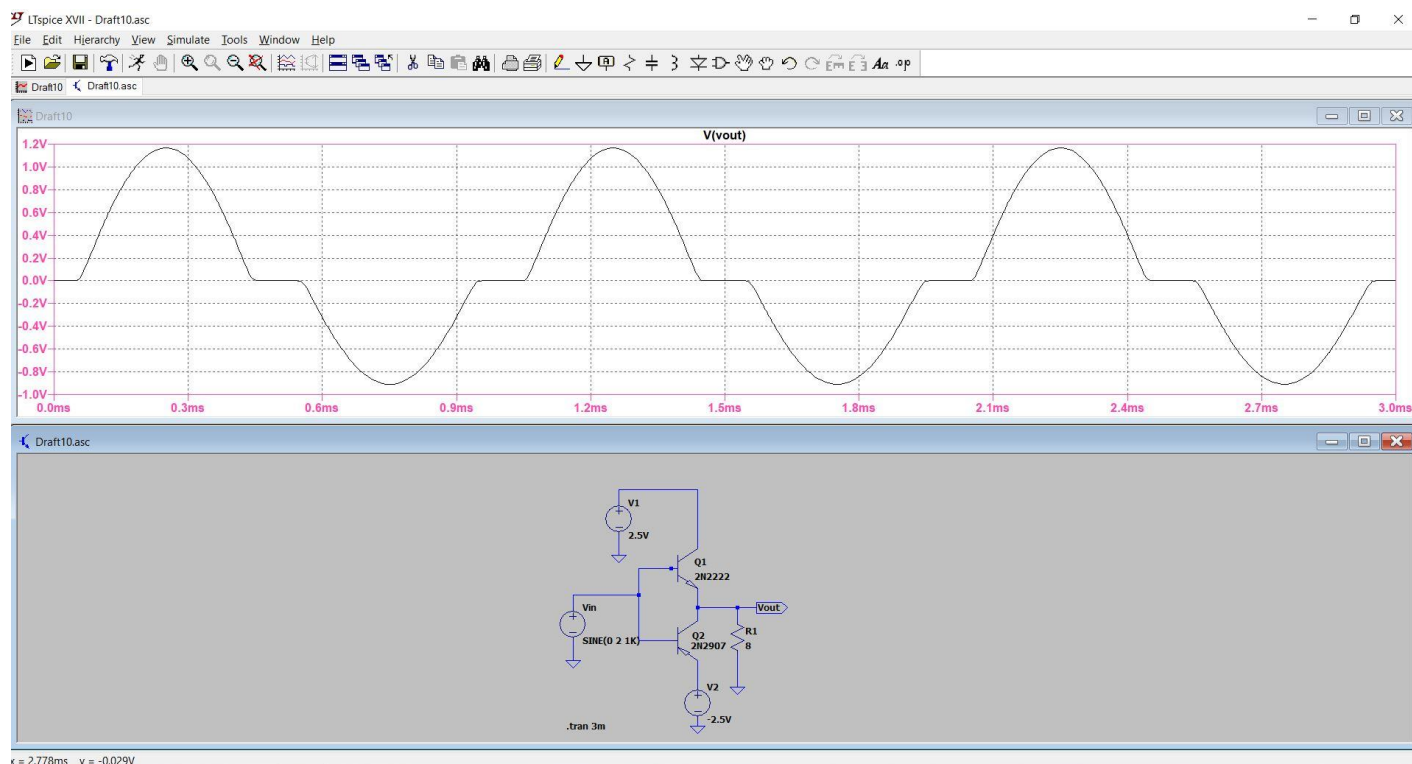

### b) When $R = 16\text{ ohms}$

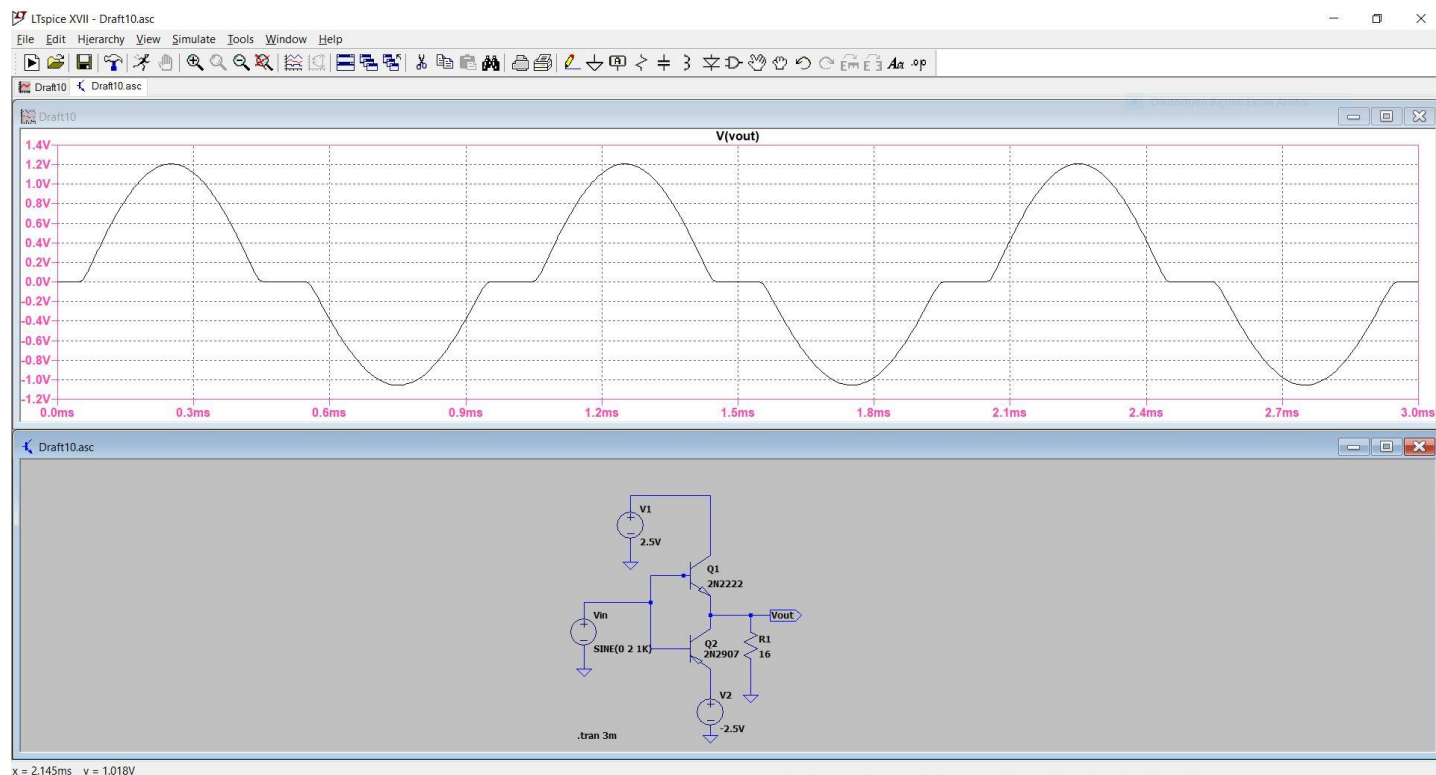

-> When the value of  $R$  increases,  $V_{out\_max}$  increases but the  $V_{out\_min}$  decreases.